

Karnaugh-map Using Arduino

SURAJIT SARKAR

sarkars531@gmail.com

IITH - FUTURE WIRELESS COMMUNICATIONS-(FWC22085)

Contents

1	Introduction
2	components
3	karnaugh-map
3.1	Implementation
4	Truthtable
5	Hardware Connections
6	Software

Abstract

The objective of this manual is to show how to verify following min-terms.

$$f(A,B,C,D) = \sum m(2, 3, 8, 10, 11, 12, 14, 15)$$

using karnaugh-map

1 Introduction

Karnaugh-map provides a systematic method for simplifying boolean expressions and may produce simplest SOP or POS expressions.

karnaugh-map used to minimize number of logic gates that are required in a digital circuit.

2 components

component	value	quantity
Arduino	UNO	1

Table-0

3 karnaugh-map

3.1 Implementation

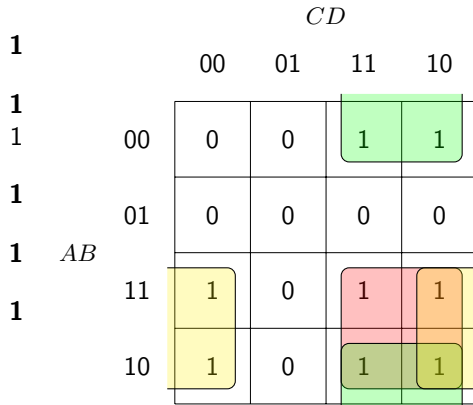


Figure 1:k-map

From the above karnaugh-map the expression is

$$f = A\bar{D} + AC + \bar{B}C$$

This karnaugh-map is verified by using

Truthtable Table-1

4 Truthtable

A	B	C	D	O/P
0	0	0	0	0
0	0	0	1	0
1	0	1	0	1
1	0	1	1	1
0	1	0	0	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1

Table-1

5 Hardware Connections

- 1.connect the arduino to the computer
- 2.The led will ON and OFF when changing the inputs .

6 Software

Download the following code

```
https://github.com/sssurajit/fwc/blob/main/codes/src/  
main.cpp
```